

# AS-00 Basic Electrical Principles

Revision sheet

## 1 Fundamental Units

There are a number of fundamental units which are used commonly across the entirety of electronics.

### 1.1 Charge

Charge ( $Q$ ) is measured in the Coulomb (C).

### 1.2 Current

Current ( $I$ ) is the amount of charge flowing past a point in a circuit per second. It is measured in Amperes, Amps for short, (A).

### 1.3 Potential Difference

Potential difference, also known as Voltage ( $V$ ), is measured in Volts (V). The potential difference between two points is defined as the energy dissipated when one coulomb of charge moves between two points. Voltage is always measured 'across' or 'between' two points.

### 1.4 Resistance

Resistance ( $R$ ) of a component depends on the resistivity of the material and its dimensions. It is measured in Ohms ( $\Omega$ ). Resistance is caused by electron collisions. A thicker wire will result in a lower resistance whereas a longer or hotter wire will result in an increased resistance.

### 1.5 Power

Power ( $P$ ) is energy transfer per second. It is measured in Watts (W). Components which remove energy from a circuit (usually resistors), are said to 'dissipate' power.

## 2 Fundamental Equations

### 2.1 Current, Charge and Time

$$\text{Current} = \frac{\text{Charge}}{\text{Time}}$$
$$I = \frac{Q}{t}$$

### 2.2 Work, Charge and Voltage

$$\text{Work} = \text{Charge} \times \text{Voltage}$$
$$W = QV$$

### 2.3 Voltage, Current and Resistance

$$\text{Voltage} = \text{Current} \times \text{Resistance}$$
$$V = IR$$

### 2.4 Power, Energy and Time

$$\text{Power} = \frac{\text{Energy}}{\text{Time}}$$
$$P = \frac{E}{T}$$

### 2.5 Power, Current and Voltage

$$\text{Power} = \text{Current} \times \text{Voltage}$$
$$P = IV$$

### 2.6 Power, Current and Resistance


$$\text{Power} = \text{Current}^2 \times \text{Resistance}$$
$$P = I^2 R$$

## 3 Circuit components

### 3.1 Resistors


Resistors are very small and come in different series. Each series has a different tolerance and different decades. For this course, use the E24 series which is listed on the front cover of the formula book. To choose resistors, generally pick the E24 resistor which has a higher resistance value than the ideal value.

### 3.2 Voltmeter

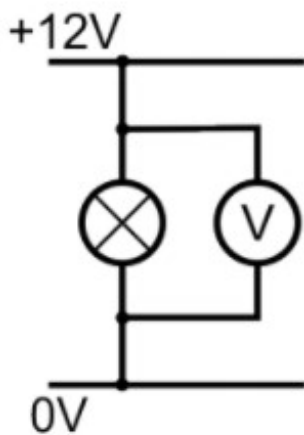


A voltmeter is connected in parallel with the component which you are measuring the voltage of.

### 4.2 Parallel

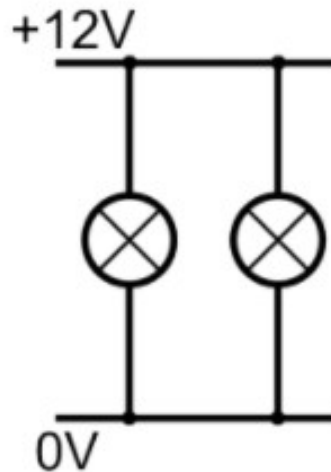

The current is split between the components. The voltage is the same across the components.


### 3.3 Ammeter

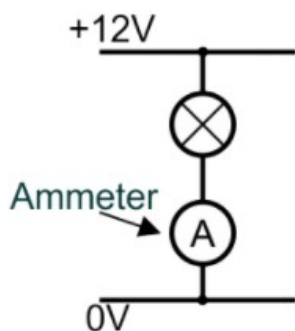

An ammeter is connected in series with the component which you are measuring the current of.


## 5 Multiple resistor circuits

### 5.1 Resistors in Series

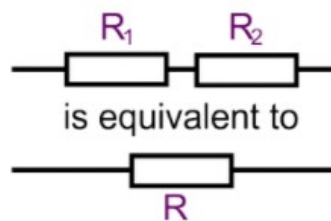

$R_{total} = R_1 + R_2 \dots$  This will work for any number of resistors.


### 5.2 Resistors in Parallel

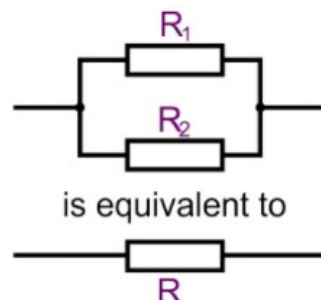

$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} \dots$  This works for any number of resistors, however if you just have two in a circuit, you can use the following formula:  
$$R_{total} = \frac{R_1 \times R_2}{R_1 + R_2}$$

## 4 Circuit Styles

### 4.1 Series

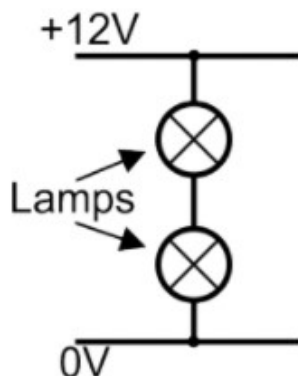


The current through the components is the same. The voltage is different across the components.

## 6 Laws

There are a number of key laws to understand with Electronics.
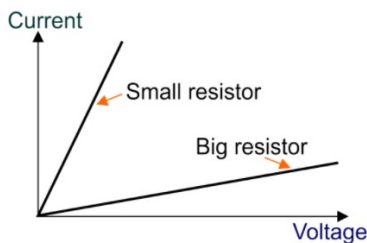
## 6.1 Ohms Law

The current through an ohmic conductor is directly proportional to the voltage at a constant temperature.




Non-Ohmic conductors have curvy lines on the graph.
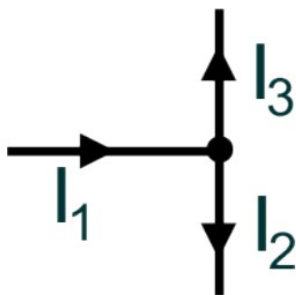
## 6.2 Kirchhoff's Current Law

*The sum of the currents flowing into a node is zero.*

Or alternatively - The sum of the currents flowing into the nodes equals the sum of those flowing out.




$$I_1 = I_2 + I_3$$
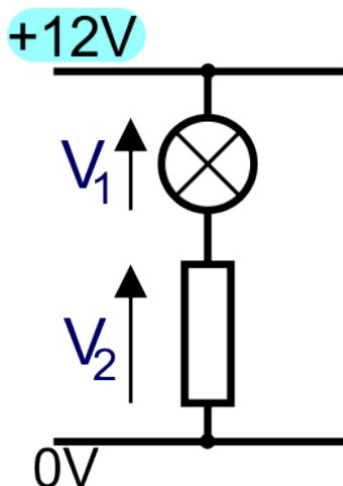
## 6.3 Kirchhoff's Voltage Law

*The sum of voltage around a closed loop is zero.*


Or alternatively - The sum of voltages across components in series is equal to the total voltage



across them.

$$V_1 + V_2 = 12V$$

## 7 Potential Dividers

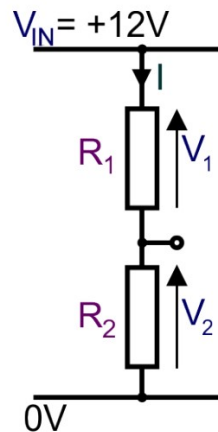

Two resistors connected in series and a power supply divides the voltage between them in the ratio of the resistors. As seen in the diagram above  $V_{IN} = V_1 + V_2$ . To work out what  $V_1$  and  $V_2$  are, use the following equations respectively

$$V_1 = \frac{R_1}{R_1 + R_2} \times V_{IN}$$

$$V_2 = \frac{R_2}{R_1 + R_2} \times V_{IN}$$


### 7.1 Potentiometers

A potentiometer is a three terminal resistor with a sliding or turning contact, that forms an adjustable voltage divider. There are two types - rotary and linear.

## 8 Sensing Circuits

Sensors are quite often needed as inputs to electronic systems. There are a few key types.


### 8.1 Light Dependent Resistor

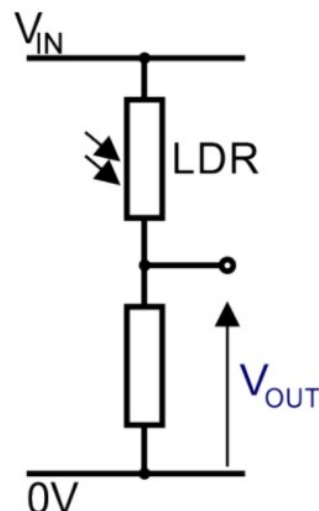

As the light levels increase, the resistance de-

creases. In the arrangement above, as the light which is shining on the LDR gets brighter,  $V_{out}$  increases. If the resistor and LDR were the other way around: as the light shining on the LDR gets brighter,  $V_{out}$  decreases.

## 8.2 Thermistor

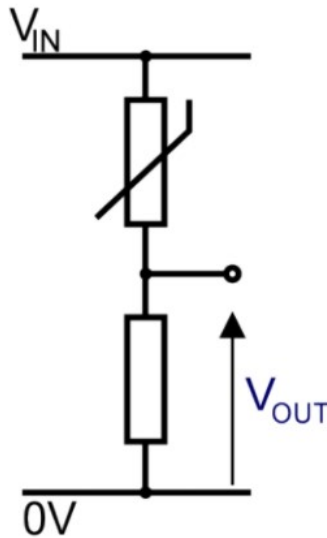

There are two types of thermistors, Negative Temperature Coefficient (NTC) and Positive Temperature Coefficient (PTC). NTC is standard and will be most commonly used.


For the diagram above, as the temperature increases,  $V_{out}$  increases. If the resistor and LDR were the other way around, as the temperature increased,  $V_{out}$  would decrease.

## 8.3 Adding a Sensitivity Control

To add a Sensitivity control, replace the fixed resistor with a variable one. By increasing the value of the variable resistor, you are decreasing the sensitivity of the circuit.
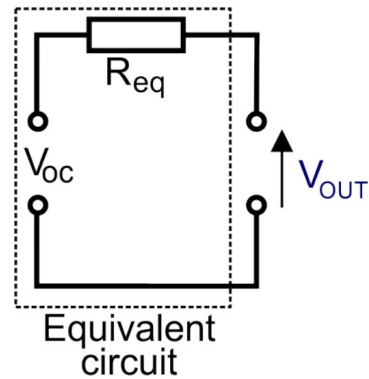
## 9 Thevenin's Theorem

Any combination of power supplies and linear components (resistors) can be replaced by a single ideal voltage source and a single ideal resistor connected in series. Thevenin's theorem is used to simplify analysis of more complicated circuits as it reduces the number of linear components. They are always drawn the same



There are a number of steps to go through to turn a circuit into a Thevenin equivalent circuit.

1. Calculate  $V_{OC}$  (Open circuit voltage which is the output voltage with no load connected).
2. Calculate  $I_{SC}$  (Short Circuit Current which is the current that flows then the output is short circuited).
3. Calculate  $R_{EQ}$  (Thevenin Resistance)

$$R_{EQ} = \frac{V_{OC}}{I_{SC}}$$

## 10 Loading

Loading is an undesirable side effect. Connecting the load causes a voltage drop, we have loaded the power supply too much for it to be able to continue to output the expected output.

When connecting a low resistance load to a voltage source, the output voltage drops (loading). To avoid this, the source resistance needs to be much lower than the load. As a general rule  $R_{LOAD} > 10 \times R_{SOURCE}$ .