

AS-3 Timing Circuits

Revision sheet

1 Capacitors



Figure 1: Circuit symbol for a capacitor

Capacitors store charge. The equation

$$Q = CV$$

can be used to calculate how much charge is stored in the capacitor. The unit of capacitance (C) is the Farad (F). Usually a capacitor will be in the region of micro/ nano/ pico farads.

1.1 Series And Parallel

The total capacitance of capacitors in series can be calculated using the following formula:

$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

The total capacitance of capacitors in parallel can be calculated using the following formula:

$$C_{total} = C_1 + C_2 + C_3 + \dots$$

1.2 Time Constant

When a resistor and capacitor are connected in series, they form a RC network. The equation $T = R \times C$ links them together, where T is the time constant and is measured in seconds.

1.3 Charging A Capacitor

The circuit below can be used to charge a capacitor.

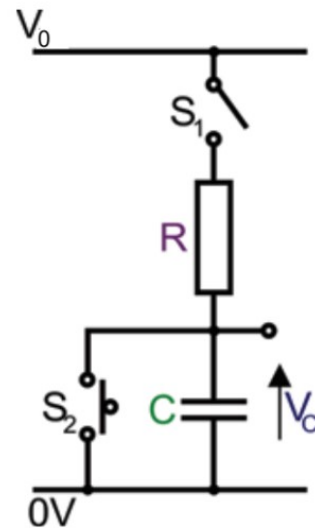


Figure 2: Circuit for charging a capacitor

We'll assume that the capacitor is initially fully discharged, therefore $V_C = 0$. When we close the switch, capacitor starts charging and current 'flows'. As the capacitor charges, the rate of charging slows down. A larger resistor will cause slower charging, therefore with 0 resistance, the capacitor would charge 'instantly'. In the diagram above, the purpose of S_2 is to discharge the capacitor so that the experiment can be repeated.

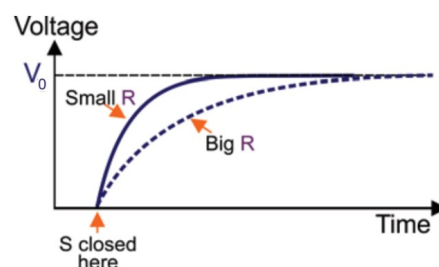


Figure 3: Graph showing voltage change over time when charging a capacitor

The equation to find the voltage over the capacitor (V_C) at a given time (t) is given below.

$$V_C = V_0 \left(1 - e^{-\frac{t}{RC}} \right)$$

The time taken to get a certain voltage over the

capacitor equation (for charging) can be seen below.

$$t = -RC \ln \left(1 - \frac{V_C}{V_0} \right)$$

1.3.1 General Rules

$V_C = 0.5V_0$ after $0.69RC$ (V_C = half the supply voltage)

$V_C \approx V_0$ (fully charged) after $5RC$.

1.4 Discharging Capacitors

The circuit below can be used to discharge a capacitor.

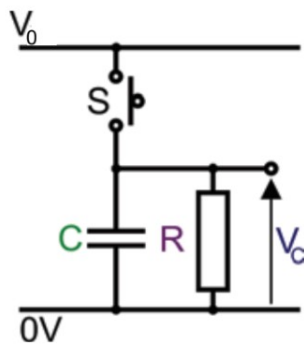


Figure 4: Circuit for discharging a capacitor

Pressing switch S instantly charges the capacitor. Discharging begins when S is released. C discharges through R .

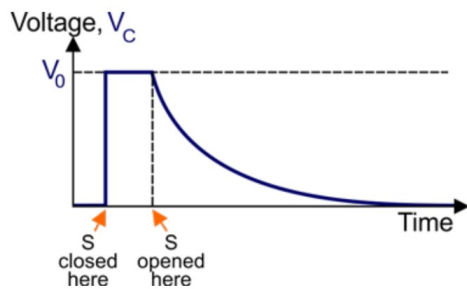


Figure 5: Graph showing voltage change over time when discharging a capacitor

The equation to find the voltage over the capacitor (V_C) at a given time (t) is given below.

$$V_C = V_0 e^{-\frac{t}{RC}}$$

The time taken to get a certain voltage over the capacitor equation (for discharging) can be seen below.

$$t = -RC \ln \left(\frac{V_C}{V_0} \right)$$

1.4.1 General Rules

$V_C = 0.5V_0$ after $0.69RC$

$V_C \approx 0V$ after $5RC$ (fully discharged)

2 Monostable Circuits

A monostable is a circuit which produces a single timing pulse. It has only one stable state; which it stays in until triggered, then it moves to the unstable state for a set period of time then returns to the stable state.

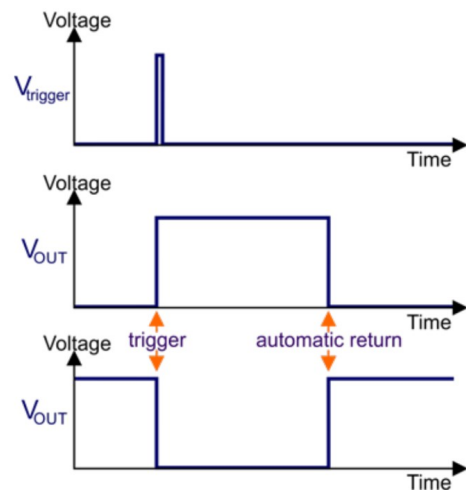


Figure 6: Monostable circuit behaviour

2.1 NOT Gate Monostable

NOT gates have something called a switching threshold - this is the point at which they will invert their input. This can be used to design a NOT gate monostable.

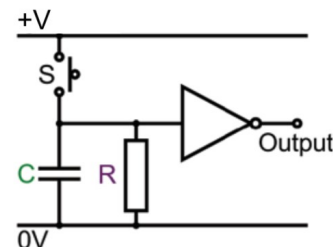


Figure 7: Circuit for a NOT gate monostable

The output of the monostable can be shown on a graph.

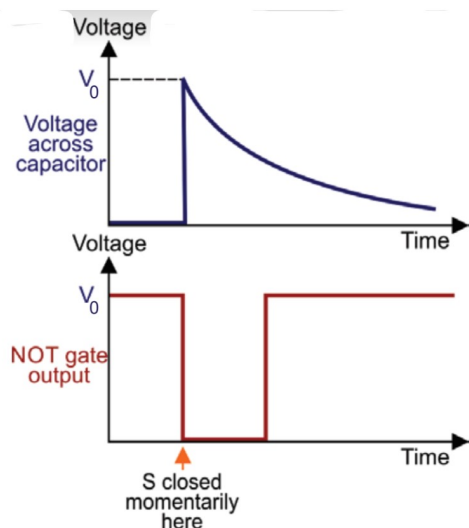


Figure 8: Graph showing the NOT gate monostable

2.1.1 Delayed Response Monostable

The resistor can be moved and another switch added which gives a circuit that produces a delay before triggering the monostable.

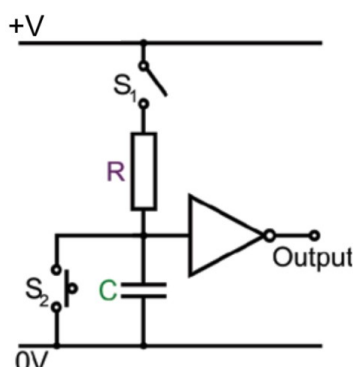


Figure 9: Circuit for a delayed NOT monostable

This gives us the following graphed output.

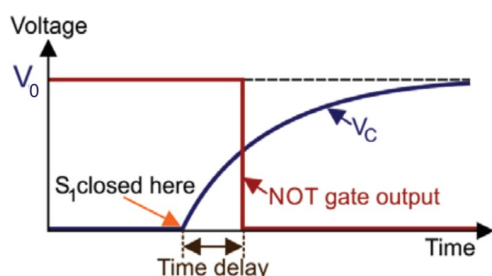


Figure 10: Graph showing the delayed NOT gate monostable

2.2 555 Timer Monostable

The 555 Timer IC can be used to build a monostable as seen below.

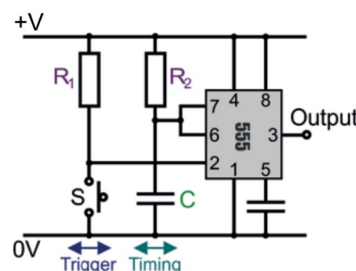


Figure 11: Circuit for a 555 timer monostable

$T = 1.1RC$ where resistor used is R_2 .

Once the button is pressed, the monostable triggers and behaves as expected. You cannot re-trigger the 555 monostable mid pulse by pressing the button down again. The output will stay high all the time the button is pressed, even if T is over.

2.3 Uses Of Monostables

Monostables can be used to de-bounce a switch.

3 Astable Circuits

These have no stable states. They oscillate between on and off. The time on (T_H) is called a Mark and the time off (T_L) is called a space. The time period can be calculated as follows:

$T = T_L + T_H$. The time on and time off do not have to be equal. The following graph shows this.

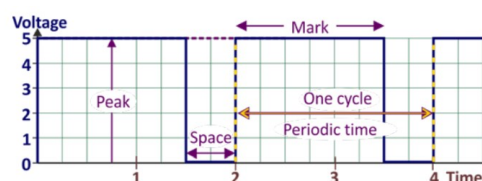


Figure 12: Graph showing the behaviour of an astable

The output is a square wave. The frequency can be calculated using the equation seen below.

$$f = \frac{1}{t} = \frac{1}{T_H + T_L}$$

3.1 Schmitt Inverter Astable

A Schmitt Inverter can be used to build an astable. It has upper and lower switching thresholds which makes it really useful for this. Its upper threshold is $\frac{2}{3}V_S$ and its lower threshold is

$\frac{1}{3}V_S$. The Schmitt Inverter Astable has the following circuit diagram.

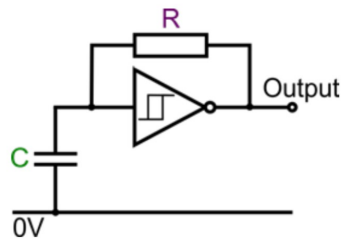


Figure 13: Circuit for a Schmitt inverter astable

This produces the following output graph.

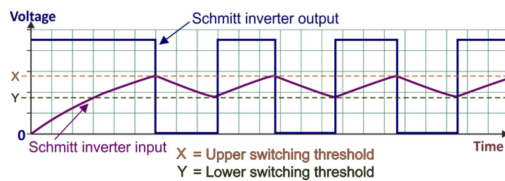


Figure 14: Graph showing the inputs, output and switching thresholds of a Schmitt inverter astable

The Mark:Space ratio will always be 1:1 and the equation for frequency is as follows.

$$f = \frac{1}{RC}$$

3.2 555 Timer Astable

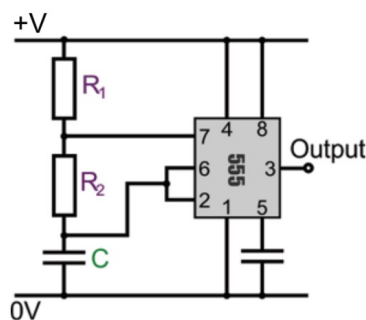


Figure 15: Circuit for a 555 timer astable

The capacitor charges through R_1 and R_2 , providing the time on

$$T_H = 0.7(R_1 + R_2)C$$

The capacitor discharges through R_2 , providing the time off

$$T_L = 0.7R_2C$$

The frequency can be calculated with the following equation

$$f = \frac{1.44}{(R_1 + 2R_2)C}$$

The Mark-Space ratio can be calculated using one

of the following equations, to one.

$$\frac{T_H}{T_L} = \frac{R_1 + R_2}{R_2} = \frac{T_{on}}{T_{off}} : 1$$

It is impossible to have a Mark-Space ratio of 1:1, however if $R_2 \gg R_1$, $\frac{T_H}{T_L}$ can be closer to 1.